
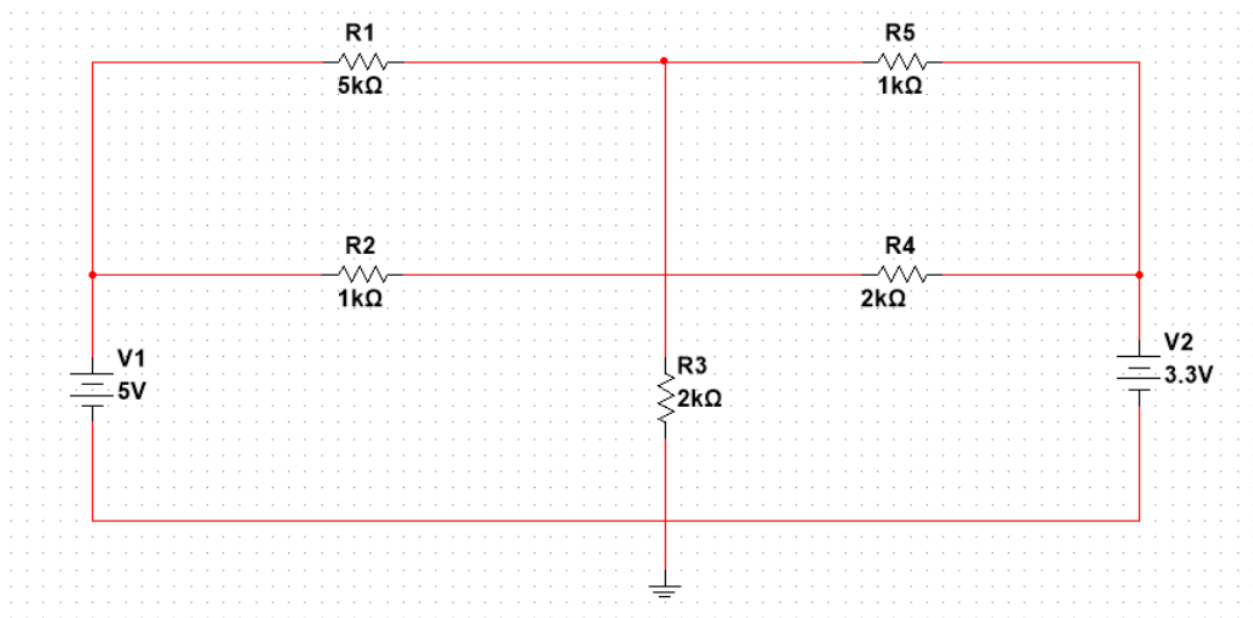



Modified Circuit:

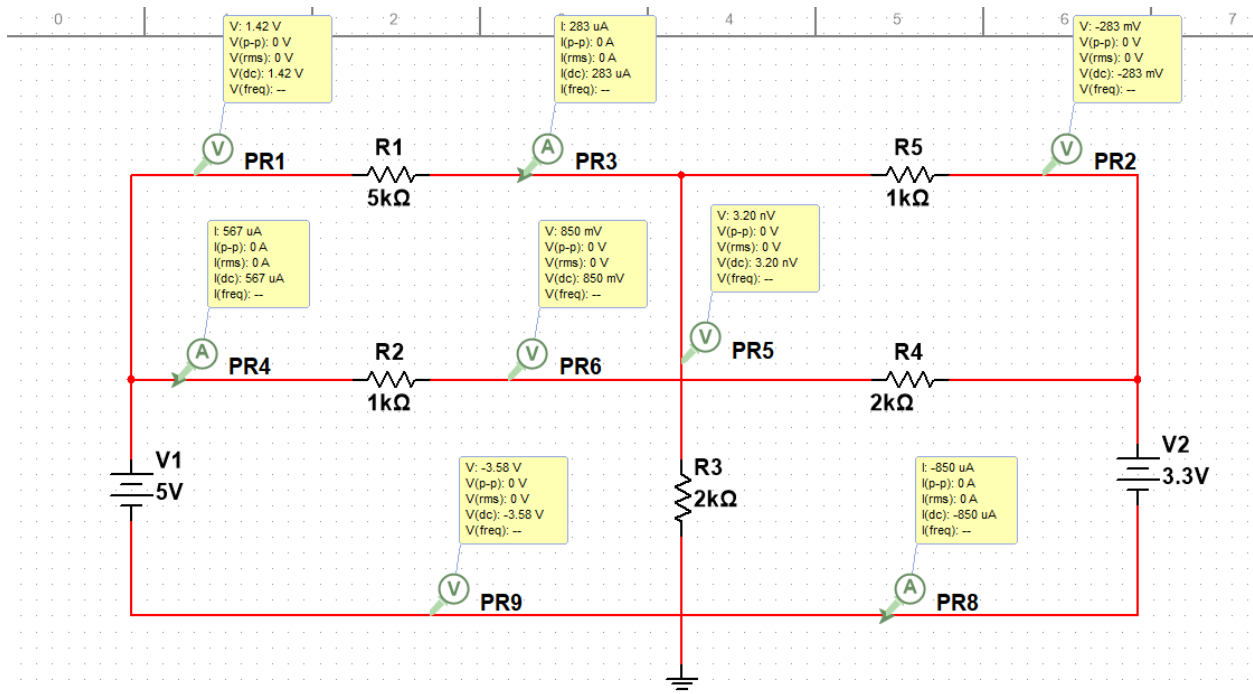

NI Multisim (with all readings):



KVL/KCL

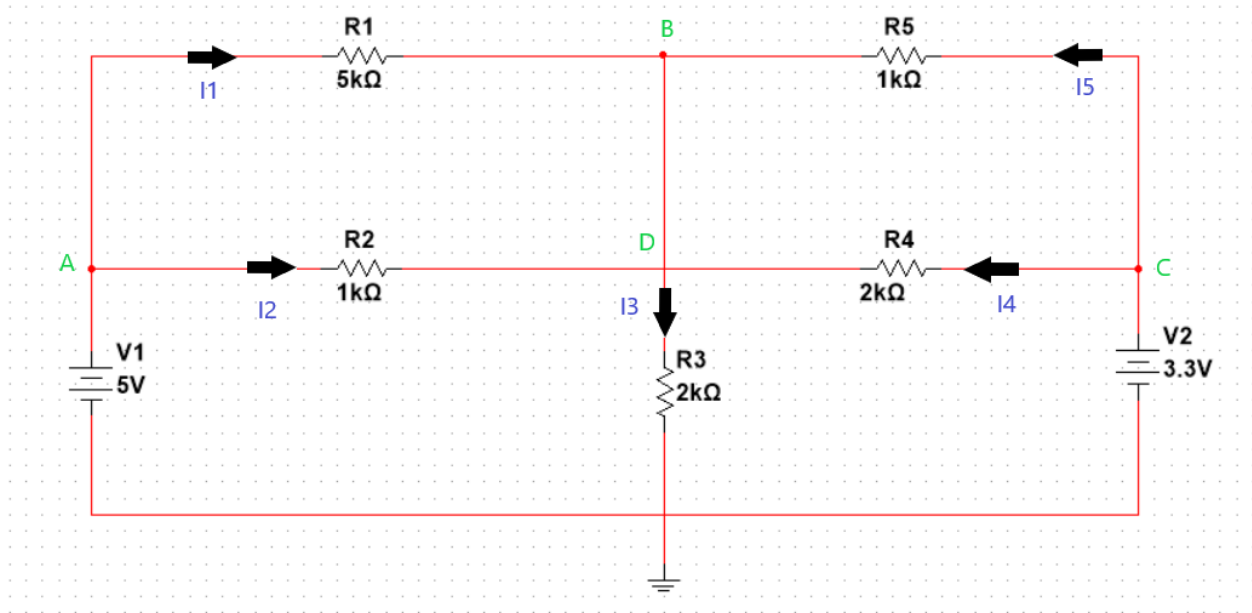

KCL at node B:

$$\sum I_{in} = \sum I_{out}$$

$$I_1 + I_5 = I_3$$

KCL at node D:

$$I_2 + I_4 = I_3$$

KVL at top-left mesh (clockwise):

$$-I_1 R_1 + I_2 R_2 = 0$$

$$-5I_1 + I_2 = 0$$

KVL at bottom-left mesh (clockwise):

$$V_1 - I_2 R_2 - I_3 R_3 = 0$$

$$5 - I_2 - 2I_3 = 0$$

KVL at top-right mesh (clockwise):

$$I_5 R_5 - I_4 R_4 = 0$$

$$I_5 - 2I_4 = 0$$


Syed Ali Zaidi
zaidis33

KVL at bottom-right mesh (clockwise):

$$I_4 R_4 - V_2 + I_3 R_3 = 0$$

$$2I_4 - 3.3 + 2I_3 = 0$$


Nodal Analysis

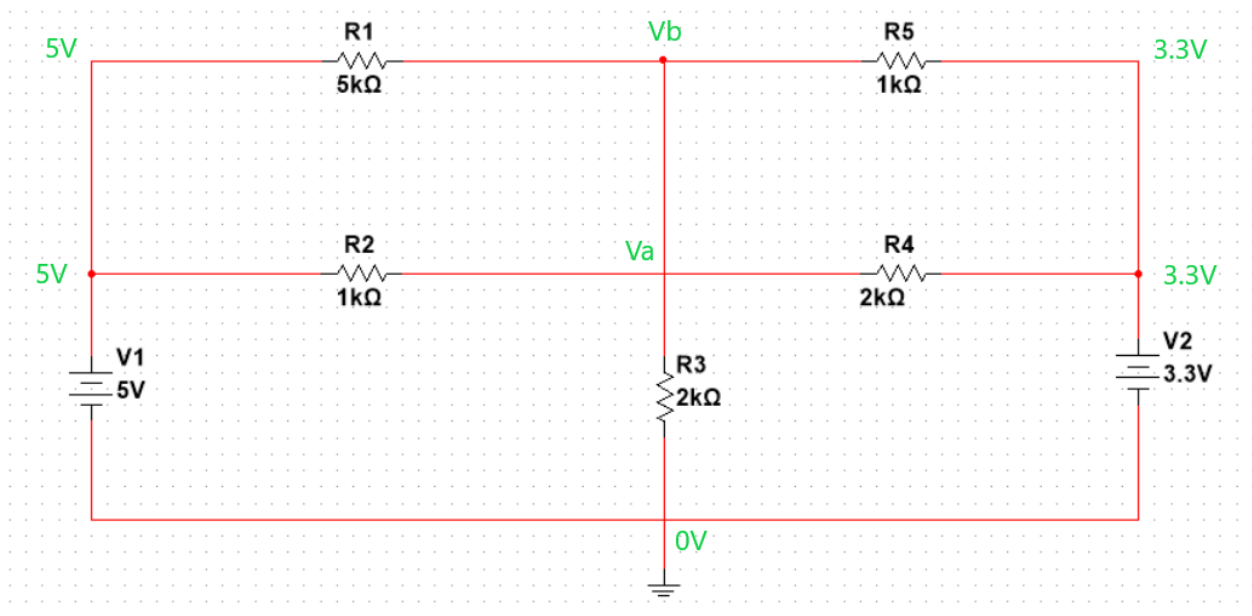

$$\begin{aligned}\text{KCL: } \sum I_{b,in} &= \sum I_{b,out} \\ \frac{5V - V_b}{5k\Omega} + \frac{3.3V - V_b}{1k\Omega} + \frac{0V - V_b}{2k\Omega} &= 0 \\ 10V - 2V_b + 33V - 10V_b - 5V_b &= 0 \\ V_b &= -2.529V\end{aligned}$$

$$\begin{aligned}\text{KCL: } \sum I_{a,in} &= \sum I_{a,out} \\ \frac{5V - V_a}{1k\Omega} + \frac{0V - V_a}{2k\Omega} + \frac{3.3V - V_a}{2k\Omega} &= 0 \\ 10V - 2V_a - V_a + 3.3V - V_a &= 0 \\ V_a &= 3.325V\end{aligned}$$

Mesh Analysis

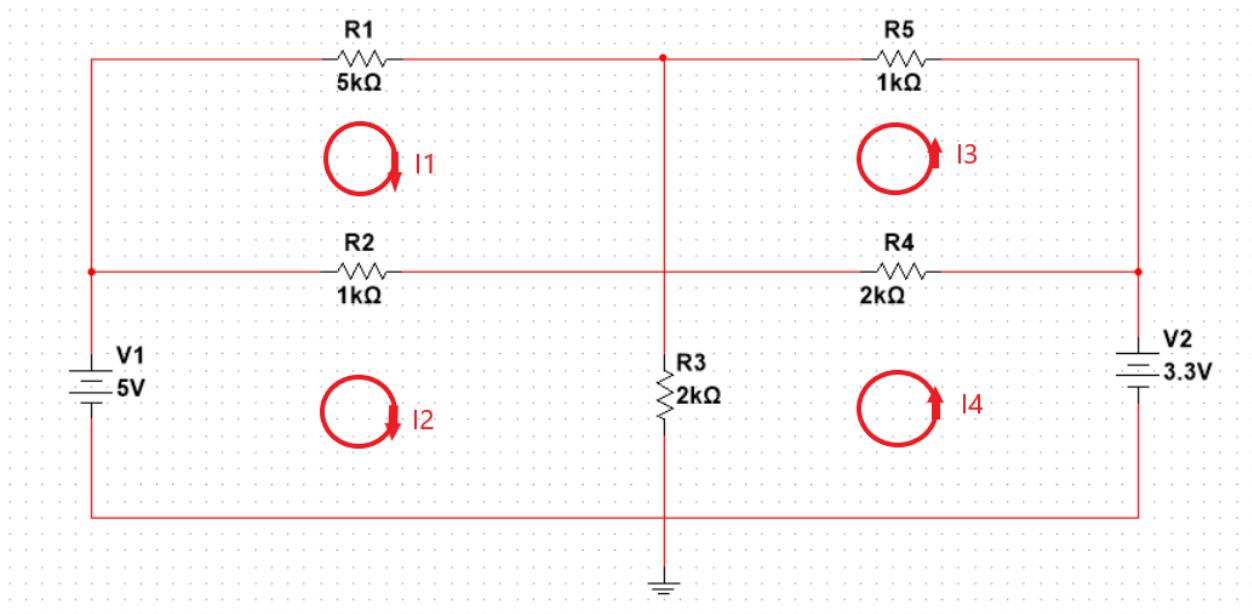

Mesh 1:

$$-I_1 R_1 - (I_1 - I_2) R_2 = 0$$

$$-5I_1 - I_1 + I_2 = 0$$

$$I_2 = 6I_1$$

Mesh 2:

$$V_1 - (I_1 - I_2) R_2 - (I_2 + I_4) R_3 = 0$$

$$5 - (I_1 - 6I_1)(1) - (6I_1 + I_4)(2) = 0$$

$$5 - 7I_1 - 2I_4 = 0$$

$$I_4 = \frac{5 - 7I_1}{2}$$

Mesh 3:

$$I_3 R_5 + (I_3 - I_4) R_4 = 0$$

$$I_3 + 2I_3 - 2I_4 = 0$$

$$3I_3 - \left(\frac{5 - 7I_1}{2} \right) = 0$$

$$6I_3 - 5 + 7I_1 = 0$$

$$I_3 = \frac{5 - 7I_1}{6}$$

Mesh 4:

$$(I_2 + I_4) R_3 + (I_3 - I_4) R_4 - 3.3 = 0$$

$$\left(6I_1 + \frac{5 - 7I_1}{2} \right) (2) + \left(\frac{5 - 7I_1}{6} - \frac{5 - 7I_1}{2} \right) (2) - 3.3 = 0$$


$$I_1 = 0.169 \text{ A}$$

$$\therefore I_2 = 6(0.169) = 1.014 \text{ A}$$

$$I_4 = 1.909 \text{ A}$$

$$I_3 = 0.636 \text{ A}$$

Superposition

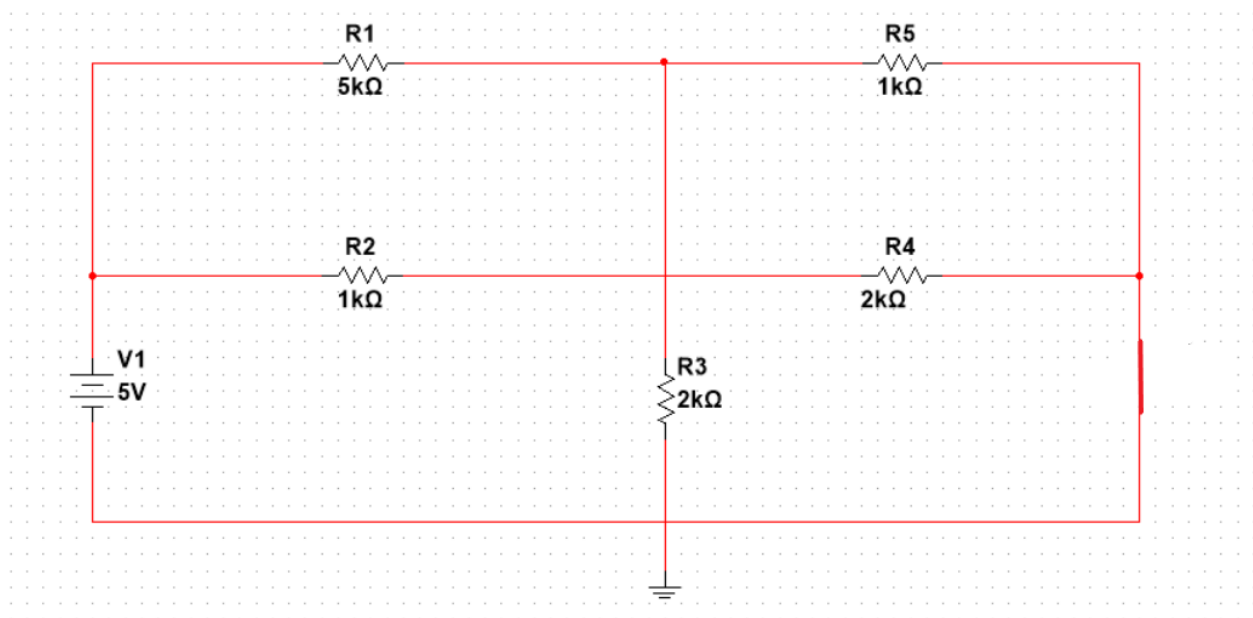

Effective Resistance of whole circuit:


$R_1 || R_2$ which is in series with $R_5 || R_4 || R_3$


$$\therefore R_{eff} = \frac{4}{3}$$

Now I don't know what to do even after plugging the values in the voltage divider equation.

Syed Ali Zaidi
zaidis33

Physical Circuit

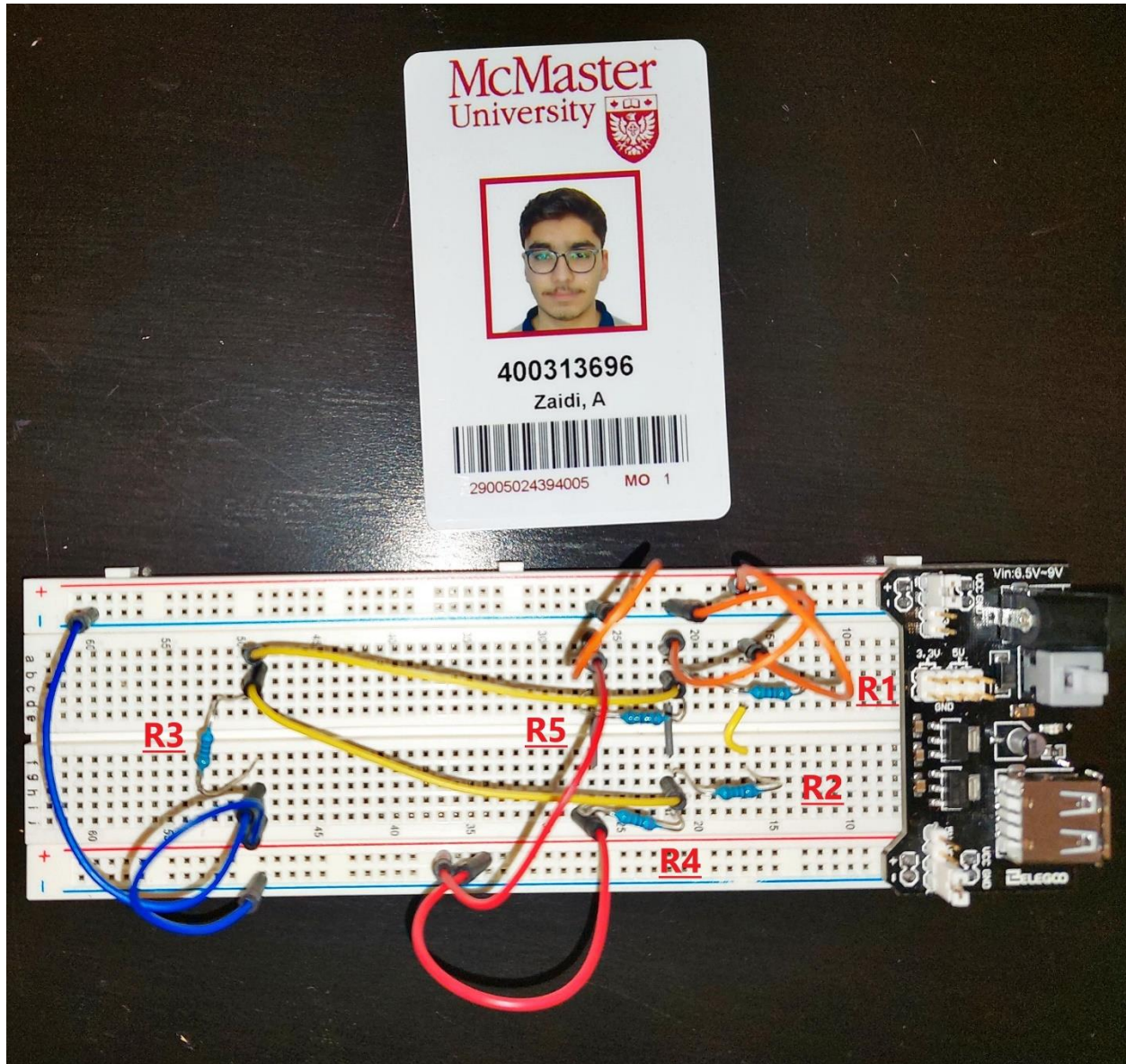

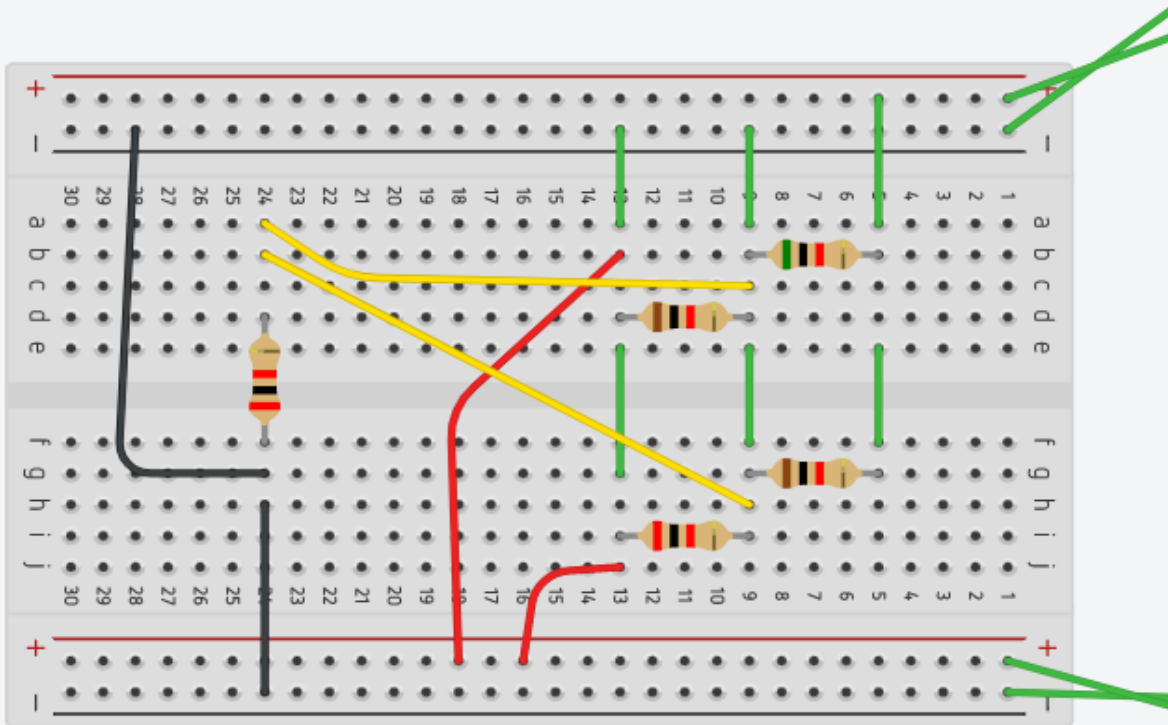

Syed Ali Zaidi
zaidis33

Measurement ($k\Omega$)	1.2% of reading ($k\Omega$)	5 of last decimal ($k\Omega$)	Total Uncertainty ($k\Omega$)
R1 = 5.070	0.06084	.5	0.56
R2 = 0.997	0.01196	.5	0.51
R3 = 2.002	0.02402	.5	0.52
R4 = 1.982	0.02378	.5	0.52
R5 = 1.000	0.01200	.5	0.51

Resistance is in the $4.000k\Omega$ range.